

Jacob Sickafoose

Lab # 4

Lab Section - 1B

2/14/2020

Description -

For this lab, we were tasked with creating a counter which counts up when you hit the up button, and counts down when you hit the down button. This counter also had to be loadable, using the 16 switches to represent the 16-bits of the counter. There were also small parts like, holding the continuous counter button only counts up until FFFC and there was btnU which only incremented up, once per button press.


Method -

I started this lab by first implementing the logic for each of the 4-bit counters. I did this by just making a truth table for the output of the 4 flip-flops when either an Up or Dw signal was set to high. These needed to output a UTC and DTC signal when they were at their highest and lowest values. The 4-bit counters finally had to handle replacing the flip-flop values with Din, if LD was high. Next I figured out how to make the 16-bit counter, using 4 of the 4-bit counters. This required utilizing the UTC and DTC signals to tell the next highest bit when to increment, or decrement. I then moved on to the edge detector which used 2 flip-flops to tell when a change from the 0 to 1 state of btnU happened. On the first change of state, it would output high for one clk cycle. Finally, I needed to make the RingCounter, Selector, and hex7seg modules for outputting the 16bit number to all 4 of the 7segment displays. Ring counter just alternated which bit of 4 was high, while selector used that as input to select which 4-bits of the 16-bit number to

upload to the display. This final 4-bit digit of the display was translated to light up the correct segments in hex7seg. The an[3:0] value was also relying on the inverse of the ring counter.

Design -

This is the schematic for my top level:

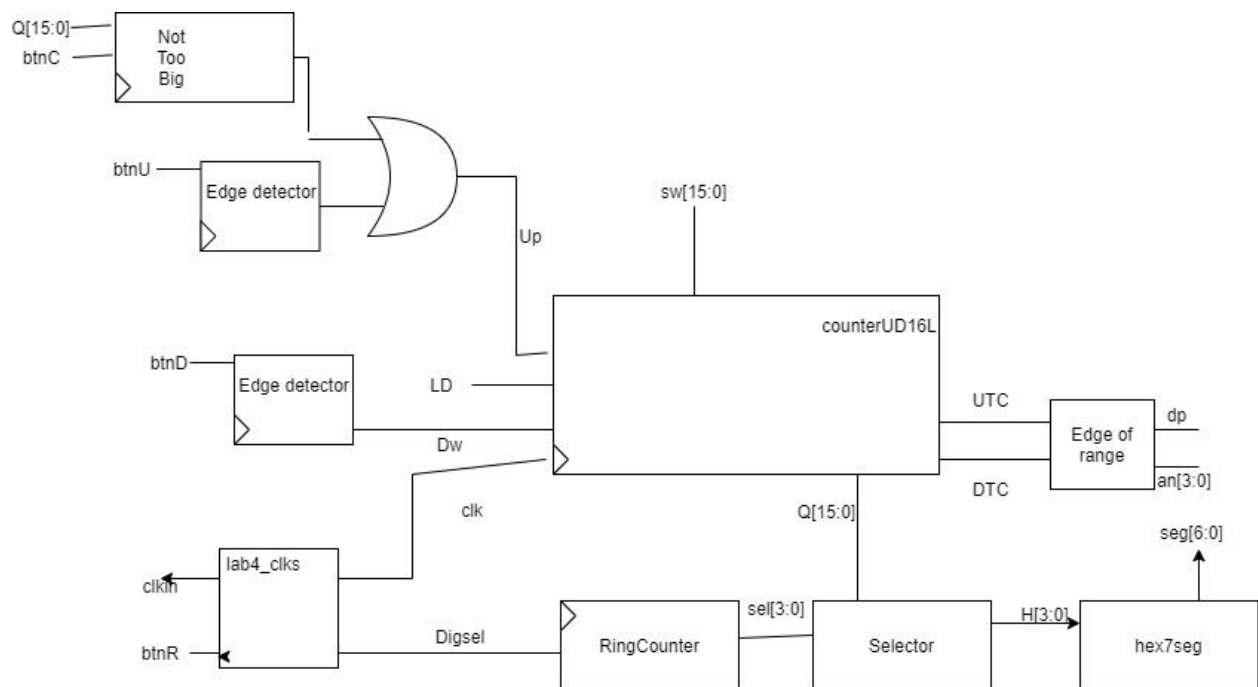

We had to figure out how to make btnC only increment until the top 14-bits of the Q[15:0] output were 1. This kept it in the range of FFFC - FFFF. We also had to turn on the left, center decimal point when the number was FFFF, and the right center point when the number was 0000. For the 4-bit counters, I used the following equation to give me the input for the flip-flops when Up or Dw were on:

$$D_0 = Q_0 \wedge Up \wedge Dw$$

$$D_1 = Q_1 \wedge (Q_0 \wedge Up) \wedge (\sim Q_0 \wedge Dw)$$

$$D_2 = Q_2 \wedge (Q_0 \wedge Q_1 \wedge Up) \wedge (\sim Q_0 \wedge \sim Q_1 \wedge Dw)$$

$$D_3 = Q_3 \wedge (Q_0 \wedge Q_1 \wedge Q_2 \wedge Up) \wedge (\sim Q_0 \wedge \sim Q_1 \wedge \sim Q_2 \wedge Dw)$$

I did a similar thing with the edge detector. I made the following truth table for the two bit flip-flops, when btn is high:

		\sim Btn		Btn	
Q_1	Q_0	D_1	D_0	D_1	D_0
0	0	0	0	0	1
0	1	1	0	1	1
1	0	0	0	0	1
1	1	1	0	1	1

Where I got the following equations for the D's:

$$D_0 = \text{btn}$$

$$D_1 = Q_0$$

Conclusion -

In order to finish this lab, I had to learn how to use flip-flops, as well as how to string them together for different effects. We had to use them to count, use them to detect edges in alternating signals, and how to make a ring counter with them. The longest part was figuring out how to make the counters and implement their truth table. It took a long time also, to string all the counters together and figure out how to use their UTC and DTC values. The rest was pretty easy to implement. If I had to do this lab again, it would be much better now that I understand how flip-flops work.

Appendix -

```

module lab4_top(
    input clkIn,
    input btnR,
    input btnU,
    input btnD,
    input btnC,
    input btnL,
    input [15:0] sw,
    output [6:0] seg,
    output dp,
    output [3:0] an,
    output [15:0] led
);

    wire dig_sel;
    wire Dw, OR1, OR2, OR3, UTC, DTC;
    wire [15:0] Q;
    wire [3:0] sel, H;
    wire clk;
    assign led = sw;

    questionMark question (.Q(Q), .btn(btnC), .out(OR1));
    lab4_clks clk (.clkIn(clkIn), .greset(btnR), .clk(clk), .digSel(dig_sel));
    edgeDetector edgeDetectorUp (.btn(btnU), .clk(clk), .btnOut(OR2));
    edgeDetector edgeDetectorDw (.btn(btnD), .clk(clk), .btnOut(Dw));
    assign OR3 = OR1 | OR2;
    counterUD16L Counter (.clk(clk), .Din(sw), .Dw(Dw), .Up(OR3), .LD(btnL),
        .UTC(UTC), .DTC(DTC), .Q(Q));
    ringCounter RingCounter (.adv(dig_sel), .clk(clk), .sel(sel));
    selector Selector (.sel(sel), .N(Q), .H(H));
    hex7seg hex7seg (.n(H), .seg(seg));

    assign an = ~sel;
    assign dp = ~(DTC & sel[1] | UTC & sel[2]);
endmodule

```

```

module questionMark(
    input [15:0] Q,
    input btn,
    output out
);

    assign out = btn & ~(Q[15:2]);
endmodule

```

```

module edgeDetector(
    input btn,
    input clk,
    output btnOut
);
    wire [1:0] D;
    wire [1:0] Q;

    assign D[0] = btn;
    assign D[1] = Q[0];

    FDRE #(.INIT(1'b0)) Q0_FF (.C(clk), .R(1'b0), .CE(1'b1), .D(D[0]), .Q(Q[0]));
    FDRE #(.INIT(1'b0)) Q1_FF (.C(clk), .R(1'b0), .CE(1'b1), .D(D[1]), .Q(Q[1]));

    assign btnOut = ~Q[1]&Q[0];
endmodule

```

```

module counterUD16L(
    input clk,
    input [15:0] Din,
    input Dw,
    input Up,
    input LD,
    output UTC,
    output DTC,
    output [15:0] Q
);
    wire [3:0] utc;
    wire [3:0] dte;

    countUD4L count0 (.Up(Up), .Dw(Dw), .LD(LD), .Din(Din[3:0]), .clk(clk), .UTC(utc[0]), .DTC(dte[0]), .Q(Q[3:0]));
    countUD4L count1 (.Up(utc[0]&Up | Up&UTC), .Dw(dte[0]&Dw | Dw&DTC), .LD(LD), .Din(Din[7:4]), .clk(clk), .UTC(utc[1]), .DTC(dte[1]), .Q(Q[7:4]));
    countUD4L count2 (.Up(utc[1]&Up&utc[0] | Up&UTC), .Dw(dte[0]&dte[1]&Dw | Dw&DTC), .LD(LD), .Din(Din[11:8]), .clk(clk), .UTC(utc[2]), .DTC(dte[2]), .Q(Q[11:8]));
    countUD4L count3 (.Up(utc[2]&Up&utc[0]&utc[1] | Up&UTC), .Dw(dte[0]&dte[1]&dte[2]&Dw | Dw&DTC), .LD(LD), .Din(Din[15:12]), .clk(clk), .UTC(utc[3]), .DTC(dte[3]), .Q(Q[15:12]));

    assign UTC = utc[0]&utc[1]&utc[2]&utc[3];
    assign DTC = dte[0]&dte[1]&dte[2]&dte[3];
endmodule

```

```

module countUD4L(
    input Up,
    input Dw,
    input LD,
    input [3:0] Din,
    input clk,
    output UTC,
    output DTC,
    output [3:0] Q
);
    wire [3:0] D;

    assign D[0] = (Q[0]^Up^Dw)&~LD | Din[0]&LD;
    assign D[1] = (Q[1]^(Q[0]&Up)^(~Q[0]&Dw))&~LD | Din[1]&LD;
    assign D[2] = (Q[2]^(Q[0]&Q[1]&Up)^(~Q[0]&~Q[1]&Dw))&~LD | Din[2]&LD;
    assign D[3] = (Q[3]^(Up&Q[2]&Q[1]&Q[0])^(Dw&~Q[2]&~Q[1]&~Q[0]))&~LD | Din[3]&LD;

    FDRE #(.INIT(1'b0)) Q0_FF (.C(clk), .R(1'b0), .CE(1'b1), .D(D[0]), .Q(Q[0]));
    FDRE #(.INIT(1'b0)) Q1_FF (.C(clk), .R(1'b0), .CE(1'b1), .D(D[1]), .Q(Q[1]));
    FDRE #(.INIT(1'b0)) Q2_FF (.C(clk), .R(1'b0), .CE(1'b1), .D(D[2]), .Q(Q[2]));
    FDRE #(.INIT(1'b0)) Q3_FF (.C(clk), .R(1'b0), .CE(1'b1), .D(D[3]), .Q(Q[3]));

    assign UTC = Q[0]&Q[1]&Q[2]&Q[3];
    assign DTC = ~Q[0]&~Q[1]&~Q[2]&~Q[3];

endmodule

```

```

module ringCounter(
    input adv,
    input clk,
    output [3:0] sel
);
    // wire [3:0] D;
    wire [3:0] Q;

    // assign D[0] = (Q[0]&~adv) | (Q[3]&adv);
    // assign D[1] = (Q[1]&~adv) | (Q[0]&adv);
    // assign D[2] = (Q[2]&~adv) | (Q[1]&adv);
    // assign D[3] = (Q[3]&~adv) | (Q[2]&adv);

    FDRE #(.INIT(1'b1)) Q0_FF (.C(clk), .R(1'b0), .CE(adv), .D(Q[3]), .Q(Q[0]));
    FDRE #(.INIT(1'b0)) Q1_FF (.C(clk), .R(1'b0), .CE(adv), .D(Q[0]), .Q(Q[1]));
    FDRE #(.INIT(1'b0)) Q2_FF (.C(clk), .R(1'b0), .CE(adv), .D(Q[1]), .Q(Q[2]));
    FDRE #(.INIT(1'b0)) Q3_FF (.C(clk), .R(1'b0), .CE(adv), .D(Q[2]), .Q(Q[3]));

    assign sel[0] = Q[0];
    assign sel[1] = Q[1];
    assign sel[2] = Q[2];
    assign sel[3] = Q[3];
endmodule

```

```

module selector(
    input [3:0] sel,
    input [15:0] N,
    output [3:0] H
);

    assign H[0] = (~sel[3]&~sel[2]&~sel[1]&sel[0]&N[0]) | (~sel[3]&~sel[2]&sel[1]&~sel[0]&N[4]) | (~sel[3]&sel[2]&~sel[1]&~sel[0]&N[8]) | (sel[3]&~sel[2]&~sel[1]&~sel[0]&N[12]);
    assign H[1] = (~sel[3]&~sel[2]&~sel[1]&sel[0]&N[1]) | (~sel[3]&~sel[2]&sel[1]&~sel[0]&N[5]) | (~sel[3]&sel[2]&~sel[1]&~sel[0]&N[9]) | (sel[3]&~sel[2]&~sel[1]&~sel[0]&N[13]);
    assign H[2] = (~sel[3]&~sel[2]&~sel[1]&sel[0]&N[2]) | (~sel[3]&~sel[2]&sel[1]&~sel[0]&N[6]) | (~sel[3]&sel[2]&~sel[1]&~sel[0]&N[10]) | (sel[3]&~sel[2]&~sel[1]&~sel[0]&N[14]);
    assign H[3] = (~sel[3]&~sel[2]&~sel[1]&sel[0]&N[3]) | (~sel[3]&~sel[2]&sel[1]&~sel[0]&N[7]) | (~sel[3]&sel[2]&~sel[1]&~sel[0]&N[11]) | (sel[3]&~sel[2]&~sel[1]&~sel[0]&N[15]);

endmodule

```

```

module m8_1(
    input [7:0] in,
    input [2:0] sel,
    output o
);

    assign o = ((~sel[2]&~sel[1]&~sel[0]&in[0]) | (~sel[2]&~sel[1]&sel[0]&in[1]) |
    (~sel[2]&sel[1]&~sel[0]&in[2]) | (~sel[2]&sel[1]&sel[0]&in[3]) | (sel[2]&~sel[1]&~sel[0]&in[4]) |
    (sel[2]&~sel[1]&sel[0]&in[5]) | (sel[2]&sel[1]&~sel[0]&in[6]) | (sel[2]&sel[1]&sel[0]&in[7]));

endmodule

```

```


module hex7seg(
    input [3:0] n,
    output [6:0] seg
);

    m8_1 a(.in({1'b0,n[0],n[0], 1'b0, 1'b0, ~n[0], 1'b0, n[0]}), .sel({n[3], n[2], n[1]}), .o(seg[0]));
    m8_1 b(.in({1'b1,~n[0],n[0], 1'b0, ~n[0], n[0], 1'b0, 1'b0}), .sel({n[3], n[2], n[1]}), .o(seg[1]));
    m8_1 c(.in({1'b1,~n[0],1'b0, 1'b0, 1'b0, 1'b0, ~n[0], 1'b0}), .sel({n[3], n[2], n[1]}), .o(seg[2]));
    m8_1 d(.in({n[0],1'b0,~n[0], n[0], n[0], ~n[0], 1'b0, n[0]}), .sel({n[3], n[2], n[1]}), .o(seg[3]));
    m8_1 e(.in({1'b0,1'b0,1'b0, n[0], n[0], 1'b1, n[0], n[0]}), .sel({n[3], n[2], n[1]}), .o(seg[4]));
    m8_1 f(.in({1'b0,n[0],1'b0, 1'b0, n[0], 1'b0, 1'b1, n[0]}), .sel({n[3], n[2], n[1]}), .o(seg[5]));
    m8_1 g(.in({1'b0,~n[0],1'b0, 1'b0, n[0], 1'b0, 1'b0, 1'b1}), .sel({n[3], n[2], n[1]}), .o(seg[6]));

endmodule

```


Lab 4

 

UP - increment
 DW - decrement
 LD - load from switches (takes precedence)
 Din - 4 bit vector loaded to FF if Load is high

UTC - (UP Terminal Count) is 1 when 1111 stored
 DTC - (Down Terminal Count) is 1 when the counter is 0000

Counter 4002	Q ₃	Q ₂	Q ₁	Q ₀	UP	down
	0	0	0	0	0	0
	0	0	0	1	0	0
	0	0	1	0	0	0
	0	0	1	1	0	0
	0	1	0	0	0	0
	0	1	0	1	0	0
	0	1	1	0	0	0
	0	1	1	1	0	0
	1	0	0	0	0	0
	1	0	0	1	0	0
	1	0	1	0	0	0
	1	0	1	1	0	0
	1	1	0	0	0	0
	1	1	0	1	0	0
	1	1	1	0	0	0
	1	1	1	1	0	0

$$D_0 = Q_0 \oplus UP \oplus DW$$

$$D_1 = Q_1 \oplus (Q_0 \cdot UP) \oplus (\bar{Q}_0 \cdot DW)$$

$$D_2 = Q_2 \oplus (UP \cdot Q_1 \cdot Q_0) \oplus (DW \cdot \bar{Q}_1 \cdot \bar{Q}_0)$$

$$D_3 = Q_3 \oplus (UP \cdot Q_2 \cdot Q_1 \cdot Q_0) \oplus (DW \cdot \bar{Q}_2 \cdot \bar{Q}_1 \cdot \bar{Q}_0)$$

Edge Detector	Q ₃	Q ₂	Q ₁	Q ₀	b1	b0	d1	d0
	0	0	0	0	0	1		
	0	1	1	0	1	1		
	1	0	0	0	0	1		
	1	1	1	0	1	1		

$$D_0 = b1n$$

$$D_1 = Q_0$$



Ring Counter

<u>Q₃ Q₂ Q₁ Q₀</u>				adv				<u>adv</u>			
0	0	0	1	0	0	1	0	0	0	0	1
0	0	1	0	0	1	0	0	0	0	1	0
0	1	0	0	1	0	0	0	0	1	0	0
1	0	0	0	0	0	0	1	1	0	0	0

$$D[0] = Q_0 \sim adv + Q_3 adv$$

$$D[1] = Q_1 \sim adv + Q_0 adv$$

$$D[2] = Q_2 \sim adv + Q_1 adv$$

$$D[3] = Q_3 \sim adv + Q_2 adv$$

16 bit Counter

when down and up, \times

$$00ab \xrightarrow{dw} a100 \rightarrow a0fe$$

Question Mark

1111	1111	1111	1100
1111	1111	1111	1101
1111	1111	1111	1110
1111	1111	1111	1111

$$Q[15:23] = 1$$

$$Q[15:23]$$



Scanned with
CamScanner

TN 6676
2/6/20 14:44
1 day later