

Jacob Sickafoose

Lab # 3

Lab Section - 1B

2/2/2020

### **Description -**

For this lab, we were asked to design another adder. This time making use of 3 different kinds of MUXs. We added the result of an 8-bit number given by the switches, and a 2 bit number given by two buttons. We then were asked to display the result on the two rightmost 7 segment displays. For this, we had to implement the logic again with MUXs and using a clock to refresh the displays.


### **Method -**

I started this lab by implementing the logic for each of the MUXs. I did this by just making a truth table for the selectors with the desired input line as the output. I then did sum of products to assign the output. Then I implemented the logic for a full adder using MUXs. I started off by making a truth table and using the two most significant bits as selectors on my m4\_1 MUX. Using one MUX as the output for sum, another for Cout. By appending 6 zero bits to the 2 bit number, I was then able to use 8 adders to add the 2, 8 bit numbers. Then I was done with the incrementer. For the hex 7 seg converter, we used a separate m8\_1 for each of the 7 segments. The 3 most significant bits of the desired 4 bit output, acted as the selector bits for the MUX with the 1 least significant bit deciding the input. I had the lower 4 bits going into one module of hex 7 seg, and the upper 4 bits going into another. The output of the two modules was then fed into our m2\_1x8 MUX which selects one of two 8 bit inputs. The selector for this MUX

was the resulting dig\_sel from the lab3\_digsel module given to us. This changes which of the two displays to update, based on our clock.

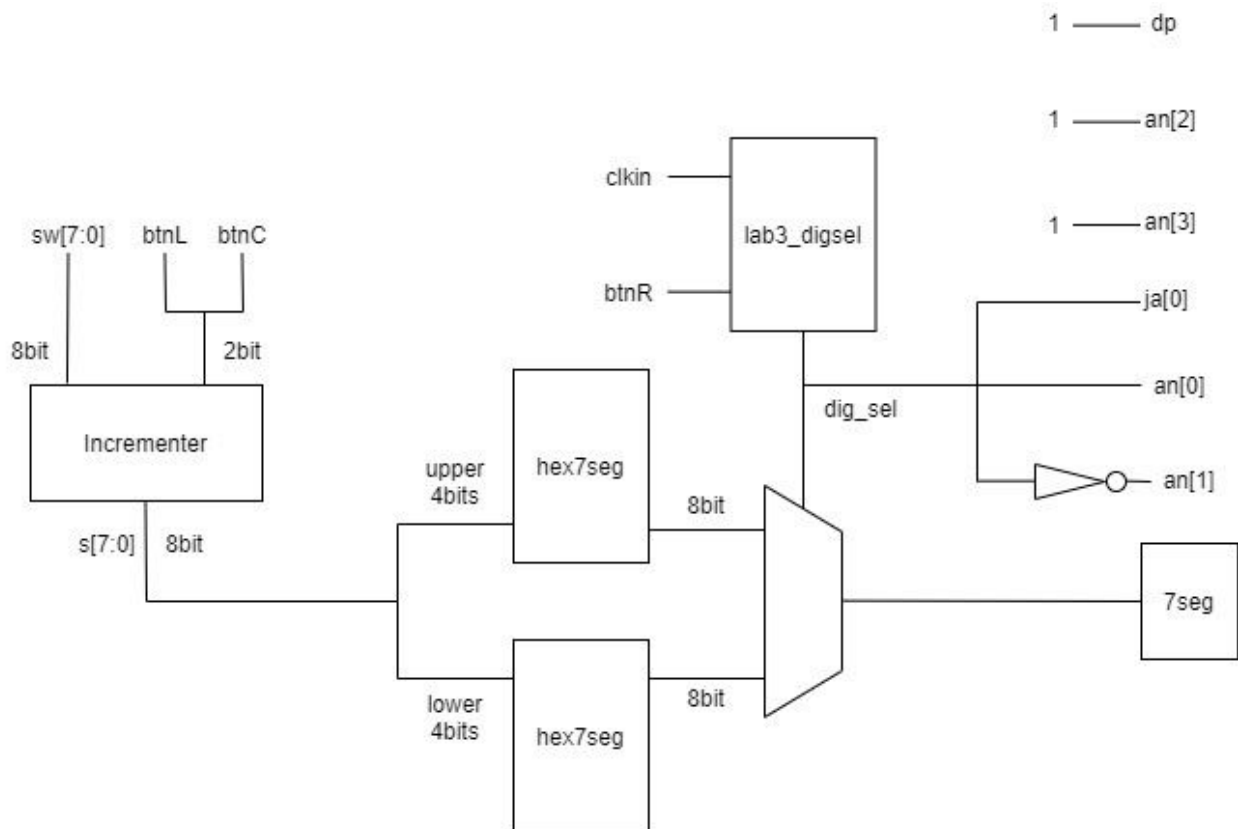
### **Design -**

This is my top level. The switches and buttons are input and added in the incrementer. The lower and upper 4 bits of output are then input into the hex7seg modules where they are converted into turning on the appropriate segments. The dig\_sel signal alternates which segment display is updated with which hex7seg module output. I also have dig\_sel going to the ja[0] pin so I could display it on the oscilloscope.




This is a schematic of the Incrementer. It just strings together all 8 adders. Adding the 2 bits of the buttons to the lower 2 bits of 8bit number the switches produce, and rippling the carry all the


way to the end.

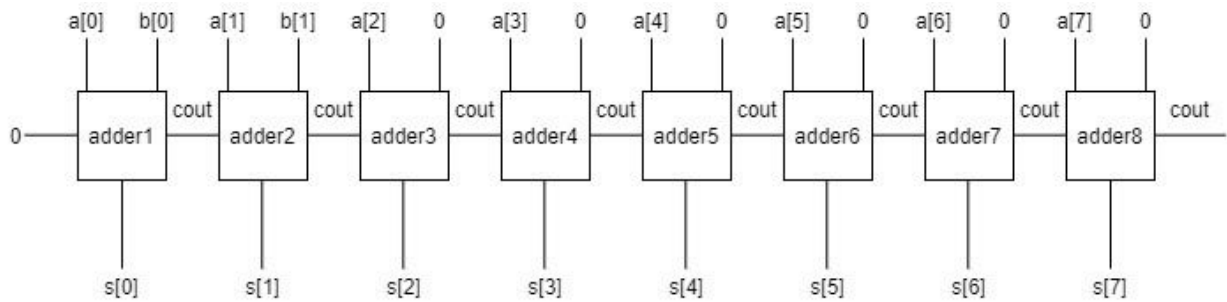

 Each of my full adders look like the following, with a and b selecting and cin as the input.



 Here is an example of one of my m8\_1 MUXs implementing the “a” segment of the 7seg display.




### **Conclusion -**


In order to finish this lab, I had to learn how to use MUXs to implement a truth table, as well as how to program MUXs in Verilog. I also had to learn how to use buses in Verilog. I also learned how to use the clock to update the displays. I also learned how to output a signal to a JA pin on the board, as well as how to use the simulation. If I had to do that lab again, it would be alot easier as I am much better at implementing truth tables with MUXs as well as using buses. I also messed up on the full adder and swapped my sum and cout results, costing me a lot of time.
 
### **Appendix -**

The output of dig\_sel on the oscilloscope:



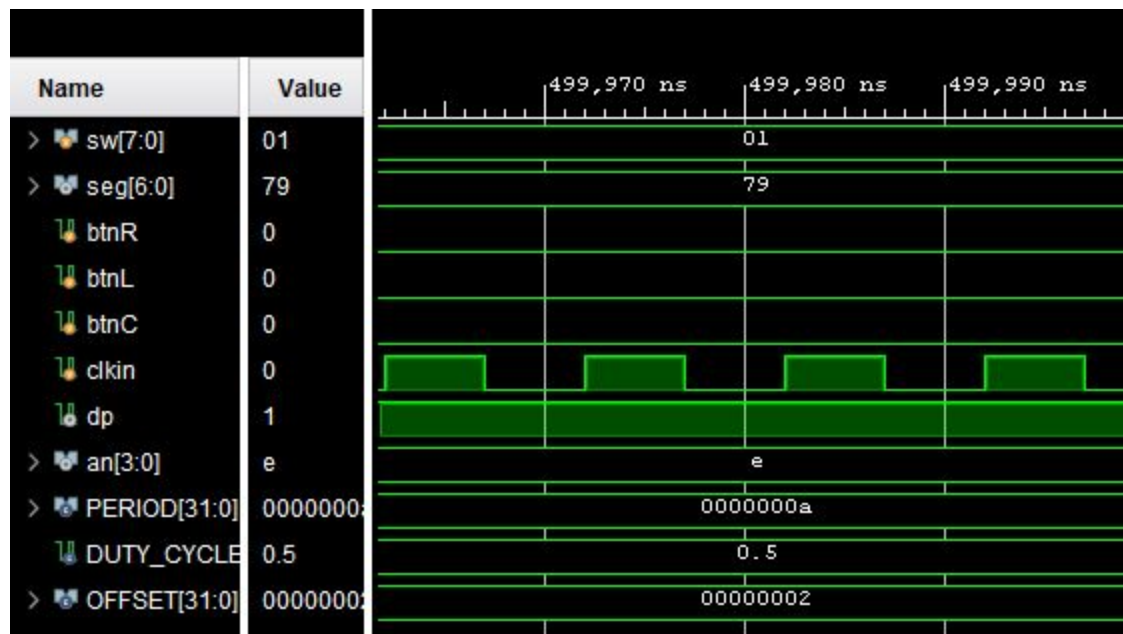The simulation, which I used to find out that my sum and cout MUXs were swapped:



Top level:

```

module lab3_top(
    input [7:0] sw,
    input btnL,
    input btnC,
    input btnR,
    input clkin,
    output [6:0] seg,
    output dp,
    output [3:0] an,
    output JA
);

    wire [7:0] s;
    wire [6:0] hex1;
    wire [6:0] hex2;
    wire dig_sel;
    wire [7:0] temp;

    lab3_digsel digsel(.clkin(clkin), .greset(btnR), .digsel(dig_sel));
    incrementer incrementer(.a(sw), .b({btnL, btnC}), /*outputs*/.s(s));

    hex7seg hex7seg1(.n(s[3:0]), /*outputs*/ .seg(hex1));
    hex7seg hex7seg2(.n(s[7:4]), /*outputs*/ .seg(hex2));

    m2_lx8 mux(.in0({1'b0, hex1}), .in1({1'b0, hex2}), .sel(dig_sel), .o(temp));
    assign seg = temp[6:0];
    assign dp = 1'b1;
    assign an[0] = dig_sel/*1'b0*/;
    assign an[1] = ~dig_sel/*1'b1*/;
    assign an[2] = 1'b1;
    assign an[3] = 1'b1;
    assign JA = dig_sel;

endmodule

```

```

module incrementer(
    input [7:0] a,
    input [1:0] b,
    output [7:0] s
);
    wire c1, c2, c3, c4, c5, c6, c7, c8;
    fullAdder adder1(.a(a[0]), .b(b[0]), .cin(1'b0), .s(s[0]), .cout(c1));
    fullAdder adder2(.a(a[1]), .b(b[1]), .cin(c1), .s(s[1]), .cout(c2));
    fullAdder adder3(.a(a[2]), .b(1'b0), .cin(c2), .s(s[2]), .cout(c3));
    fullAdder adder4(.a(a[3]), .b(1'b0), .cin(c3), .s(s[3]), .cout(c4));
    fullAdder adder5(.a(a[4]), .b(1'b0), .cin(c4), .s(s[4]), .cout(c5));
    fullAdder adder6(.a(a[5]), .b(1'b0), .cin(c5), .s(s[5]), .cout(c6));
    fullAdder adder7(.a(a[6]), .b(1'b0), .cin(c6), .s(s[6]), .cout(c7));
    fullAdder adder8(.a(a[7]), .b(1'b0), .cin(c7), .s(s[7]), .cout(c8));
endmodule

```

```

module fullAdder(
    input a,
    input b,
    input cin,
    output s,
    output cout
);
    m4_1 sum(.in({cin, ~cin, ~cin, cin}), .sel({a, b}), .o(s));
    m4_1 carry(.in({1'b1, cin, cin, 1'b0}), .sel({a, b}), .o(cout));
endmodule

```

```

module m4_1(
    input [3:0] in,
    input [1:0] sel,
    output o
);
    assign o = ((~sel[1]&~sel[0]&in[0]) | (~sel[1]&sel[0]&in[1]) | (sel[1]&~sel[0]&in[2]) | (sel[1]&sel[0]&in[3]));
    //assign o = in[sel];
endmodule

```



```

module hex7seg(
    input [3:0] n,
    output [6:0] seg
);

    m8_l a(.in({1'b0,n[0],n[0], 1'b0, 1'b0, ~n[0], 1'b0, n[0]}), .sel({n[3], n[2], n[1]}), .o(seg[0]));
    m8_l b(.in({1'b1,~n[0],n[0], 1'b0, ~n[0], n[0], 1'b0, 1'b0}), .sel({n[3], n[2], n[1]}), .o(seg[1]));
    m8_l c(.in({1'b1,~n[0],1'b0, 1'b0, 1'b0, 1'b0, ~n[0], 1'b0}), .sel({n[3], n[2], n[1]}), .o(seg[2]));
    m8_l d(.in({n[0],1'b0,~n[0], n[0], n[0], ~n[0], 1'b0, n[0]}), .sel({n[3], n[2], n[1]}), .o(seg[3]));
    m8_l e(.in({1'b0,1'b0,1'b0, n[0], n[0], 1'b1, n[0], n[0]}), .sel({n[3], n[2], n[1]}), .o(seg[4]));
    m8_l f(.in({1'b0,n[0],1'b0, 1'b0, n[0], 1'b0, 1'b1, n[0]}), .sel({n[3], n[2], n[1]}), .o(seg[5]));
    m8_l g(.in({1'b0,~n[0],1'b0, 1'b0, n[0], 1'b0, 1'b0, 1'b1}), .sel({n[3], n[2], n[1]}), .o(seg[6]));
endmodule

```

```

module m8_l(
    input [7:0] in,
    input [2:0] sel,
    output o
);

    assign o = ((~sel[2]&~sel[1]&~sel[0]&in[0]) | (~sel[2]&~sel[1]&sel[0]&in[1]) | (~sel[2]&sel[1]&~sel[0]&in[2]) | (~sel[2]&sel[1]&sel[0]&in[3]) |
    (sel[2]&~sel[1]&~sel[0]&in[4]) | (sel[2]&~sel[1]&sel[0]&in[5]) | (sel[2]&sel[1]&~sel[0]&in[6]) | (sel[2]&sel[1]&sel[0]&in[7]));
    // assign o = in[sel];
endmodule

```

```

module m2_lx8(
    input [7:0] in0,
    input [7:0] in1,
    input sel,
    output [7:0] o
);

    assign o = {8{~sel}}&in0 | {8{sel}}&in1;
endmodule

```



b 100

7 3 1  
0

111 011 1

c 12:

7 4 1

111 100 1

d 13:

7 5 1

111 101 1

e 14:

7 6 1


111 110 1

f 15:

7 7 1  
111 111 1

 
### Lab #3

For this lab, we are making an adder, to add sw0-sw7, an 8-bit number, to a 2-bit number b+nC



Full Adder Truth Table

A	B	Cin	Sum	Cout
0	0	0		
0	0	1	1	
0	1	0	1	
0	1	1	1	
1	0	0	1	
1	0	1	1	
1	1	0	1	
1	1	1	1	1

 

A, being our 8-bit number  
B, being our 2-bit number

m8\_1

Sel0	Sel1	Sel2	in
0	0	0	in0
0	0	1	in1
0	1	0	in2
0	1	1	in3
1	0	0	in4
1	0	1	in5
1	1	0	in6
1	1	1	in7

m4\_1

Sel0	Sel1	in
0	0	in0
0	1	in1
1	0	in2
1	1	in3

00000000  
11111100

AG  
7139  
1:16PM  
1/24/20

# 7 seg display Truth table

n3	n2	n1	n0	a	b	c	d	e	f	g
0	0	0	0	$\overline{n_0}$	0	0	$\overline{n_0}$	$\overline{n_0}$	$\overline{n_0}$	1
0	0	0	1	0	0	$\overline{n_0}$	0	$\overline{n_0}$	1	1
0	0	1	0	0	0	$\overline{n_0}$	0	$\overline{n_0}$	1	0
0	0	1	1	$\overline{n_0}$	$\overline{n_0}$	0	$\overline{n_0}$	1	0	0
0	1	0	0	0	$\overline{n_0}$	0	$\overline{n_0}$	$\overline{n_0}$	$\overline{n_0}$	$\overline{n_0}$
0	1	0	1	0	$\overline{n_0}$	0	$\overline{n_0}$	$\overline{n_0}$	$\overline{n_0}$	$\overline{n_0}$
0	1	1	0	0	$\overline{n_0}$	0	$\overline{n_0}$	$\overline{n_0}$	$\overline{n_0}$	$\overline{n_0}$
0	1	1	1	0	$\overline{n_0}$	0	$\overline{n_0}$	$\overline{n_0}$	$\overline{n_0}$	$\overline{n_0}$
1	0	0	0	0	0	0	$\overline{n_0}$	$\overline{n_0}$	0	0
1	0	0	1	0	0	0	$\overline{n_0}$	$\overline{n_0}$	0	0
1	0	1	0	$\overline{n_0}$	$\overline{n_0}$	0	$\overline{n_0}$	0	0	0
1	0	1	1	$\overline{n_0}$	$\overline{n_0}$	0	$\overline{n_0}$	0	0	0
1	1	0	0	$\overline{n_0}$	$\overline{n_0}$	$\overline{n_0}$	0	0	$\overline{n_0}$	$\overline{n_0}$
1	1	0	1	$\overline{n_0}$	$\overline{n_0}$	$\overline{n_0}$	0	0	$\overline{n_0}$	$\overline{n_0}$
1	1	1	0	0	1	1	$\overline{n_0}$	0	0	0
1	1	1	1	0	1	1	1	0	0	0

